

E6201 HW6 - Solutions

$$1) \lim_{t \rightarrow \infty} \frac{t^n}{e^{st}} = \lim_{t \rightarrow \infty} \frac{nt^{n-1}}{se^{st}} = \dots = \lim_{t \rightarrow \infty} \frac{n!}{s^n e^{st}} = 0.$$

$$\Rightarrow \int_0^{\infty} t^n e^{-st} dt = -\frac{t^n}{s} e^{-st} \Big|_0^{\infty} + \frac{1}{s} \int_0^{\infty} n t^{n-1} e^{-st} dt$$

$$= n s^{-1} \int_0^{\infty} t^{n-1} e^{-st} dt = \dots = n! s^{-n-1}$$

by assumption, $\exists \varepsilon > 0$ s.t.

$$x(t) = \sum_{n=0}^{\infty} \frac{x^{(n)}(0)}{n!} t^n, \quad t \in (-\varepsilon, \varepsilon)$$

$$\Rightarrow X(s) = \sum_{n=0}^{\infty} \frac{x^{(n)}(0)}{s^{n+1}}$$

$$2) y^{(2)}(0) = y^{(1)}(0) = y(0) = u^{(1)}(0) = u(0) \Rightarrow$$

$$(s^3 + a_1 s^2 + a_2 s + a_3) Y(s) = (b_1 s^2 + b_2 s + b_3) U(s)$$

$$\Rightarrow H(s) = \frac{Y(s)}{U(s)} = \frac{b_1 s^2 + b_2 s + b_3}{s^3 + a_1 s^2 + a_2 s + a_3}$$

$$3) X(s) = (sI - A)^{-1} [b U(s) + x(0)], \quad Y(s) = c^T X(s)$$


$$\Rightarrow H(s) = c^T (sI - A)^{-1} b = \frac{c^T \text{Adj}(sI - A) b}{\det(sI - A)}$$

$$4) (sI - A_c)^{-1} b_c = \frac{[s^{n-1} \ s^{n-2} \ \dots \ 1]^T}{a(s)}$$

$$\Rightarrow H(s) = \frac{c_c^T (sI - A_c)^{-1} b_c}{a(s)} = \frac{b_1 s^{n-1} + b_2 s^{n-2} + \dots + b_n}{s^n + a_1 s^{n-1} + \dots + a_n}$$

5) 2.2-22 and 2.2-23 attached.

2.2-22

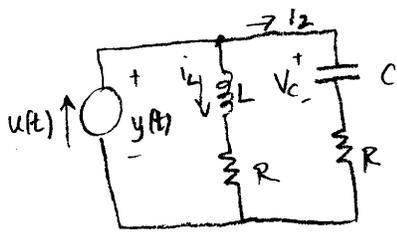

$$x_1(t) = i_L(t)$$

$$x_2(t) = V_C(t) = C^{-1} \int_0^t i_2(t) dt$$

$$\dot{x}_2 = C^{-1} i_2 = C^{-1} (u - x_1)$$

a) $V_L = L \frac{di_L}{dt} = L \dot{x}_1$ $u(t) = i_L + i_2 = x_1 + i_2$

$$i_L R + V_L - V_C - i_2 R = 0 \quad i_2 = u - x_1$$

$$R x_1 + L \dot{x}_1 - x_2 - (u - x_1) R = 0$$

$$\dot{x}_1 = \frac{-2R x_1 + x_2 + R u}{L} \Rightarrow \begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -\frac{2R}{L} & 1/L \\ -C^{-1} & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} R/L \\ C^{-1} \end{bmatrix} u$$

$$y = x_2 + (u - x_1) R = \begin{bmatrix} -R & 1 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + R u$$

b) $H(s) = c^T (sI - A)^{-1} b + d$

$$(sI - A)^{-1} = \begin{bmatrix} s + \frac{2R}{L} & -1/L \\ 1/C & s \end{bmatrix}^{-1} = \frac{1}{s(s + \frac{2R}{L}) + \frac{1}{LC}} \begin{bmatrix} s & 1/L \\ -1/C & s + \frac{2R}{L} \end{bmatrix}$$

$$c^T (sI - A)^{-1} b = \frac{\begin{bmatrix} -R & 1 \end{bmatrix}}{s(s + \frac{2R}{L}) + \frac{1}{LC}} \begin{bmatrix} s/L + 1/LC \\ -R/LC + s + \frac{2R}{L} \end{bmatrix} = \frac{-\frac{SR^2}{L} - \frac{R}{LC} - \frac{R}{LC} + \frac{S}{C} + \frac{2R}{LC}}{s(s + \frac{2R}{L}) + \frac{1}{LC}}$$

$$\Rightarrow H(s) = \frac{R(s^2 + \frac{2RS}{L} + \frac{1}{LC}) - \frac{SR^2}{L} + \frac{S}{C}}{s^2 + \frac{2RS}{L} + \frac{1}{LC}}$$

$$= \frac{Rs^2 + \frac{R^2S}{L} + \frac{S}{C} + \frac{R}{LC}}{s^2 + \frac{2RS}{L} + \frac{1}{LC}}$$

Note: if $R^2 = L/C$, then $H(s) = \frac{R(Rs^2 + \frac{2S}{C} + \frac{R}{LC})}{Rs^2 + \frac{2S}{C} + \frac{R}{LC}} = R$


$$\Rightarrow Y(s) = R U(s)$$

$$\Rightarrow y(t) = R u(t)$$

"constant resistance network"

Update to HW#6 solution 5b. [2.2-23]

Linear Systems
Spring 2012

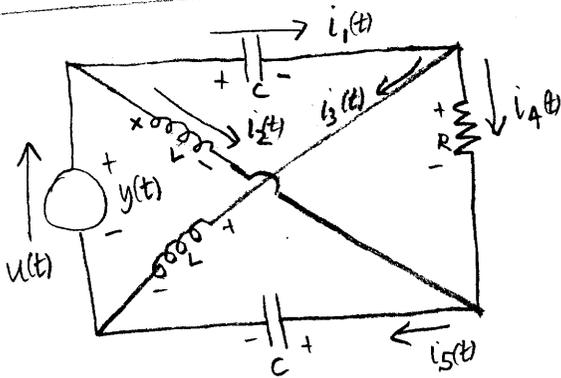

$$V_{C_1}(t) = C^{-1} \int_0^t i_1(t) dt$$

$$(1.) u = i_1 + i_2$$

$$V_{C_5}(t) = C^{-1} \int_0^t i_5(t) dt$$

$$(2.) u = i_3 + i_5$$

$$V_{L_2}(t) = L \frac{di_2(t)}{dt}$$

$$(3.) y = V_{C_1} + V_{R_4} + V_{C_5}$$

$$V_{L_3}(t) = L \frac{di_3(t)}{dt}$$

$$(4.) V_{L_3} = V_{R_4} + V_{C_5}$$

$$V_{R_4}(t) = R i_4(t)$$

$$(5.) V_{L_2} = V_{R_4} + V_{C_1}$$

$$(6.) i_1 = i_3 + i_4$$

$$x_1 = i_2 \Rightarrow \dot{x}_1 = L^{-1} V_{L_2}$$

$$x_2 = i_3 \Rightarrow \dot{x}_2 = L^{-1} V_{L_3}$$

$$x_3 = V_{C_1} \Rightarrow \dot{x}_3 = C^{-1} i_1$$

$$x_4 = V_{C_5} \Rightarrow \dot{x}_4 = C^{-1} i_5$$

$$(1) \Rightarrow \dot{x}_3 = C^{-1} u - C^{-1} x_1$$

$$(2) \Rightarrow \dot{x}_4 = C^{-1} u - C^{-1} x_2$$

$$(6) \Rightarrow V_{R_4} = R(i_1 - i_3) = (C\dot{x}_3 - x_2)R \\ = R u - R x_1 - R x_2$$

$$(3) \Rightarrow y = x_3 + R u - R x_1 - R x_2 + x_4$$

$$(4) \Rightarrow \dot{x}_2 = L^{-1} (x_4 + R u - R x_1 - R x_2)$$

$$(5) \Rightarrow \dot{x}_1 = L^{-1} (x_3 + R u - R x_1 - R x_2)$$

$$\dot{\underline{x}} = \begin{bmatrix} -L^{-1}R & -L^{-1}R & L^{-1} & 0 \\ -L^{-1}R & -L^{-1}R & 0 & L^{-1} \\ -C^{-1} & 0 & 0 & 0 \\ 0 & -C^{-1} & 0 & 0 \end{bmatrix} \underline{x} + \begin{bmatrix} L^{-1}R \\ L^{-1}R \\ C^{-1} \\ C^{-1} \end{bmatrix} u,$$

$$y = [-R \ -R \ 1 \ 1] \underline{x} + R u$$

$$H(s) = [-R \ -R \ 1 \ 1] \begin{bmatrix} s+L^{-1}R & L^{-1}R & -L^{-1} & 0 \\ L^{-1}R & s+L^{-1}R & 0 & -L^{-1} \\ C^{-1} & 0 & s & 0 \\ 0 & C^{-1} & 0 & s \end{bmatrix}^{-1} \begin{bmatrix} L^{-1}R \\ L^{-1}R \\ C^{-1} \\ C^{-1} \end{bmatrix} + R$$

$$= \frac{2(L - CR^2)s}{1 + Cs(2R + Ls)} + R$$

$$L = CR^2 \Rightarrow H(s) = R$$